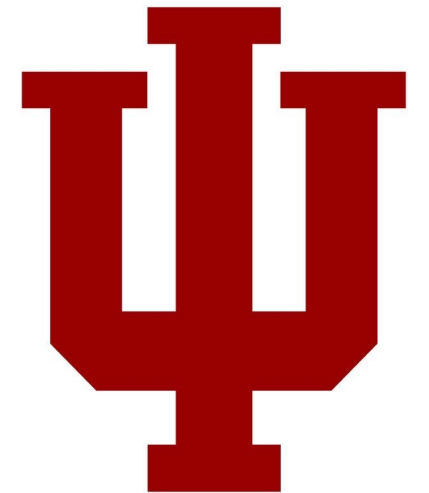


03: Bus Interfaces

Engr 315: Hardware / Software Codesign
Andrew Lukefahr
Indiana University



Announcements

- Slack – See Website
- Office Hours – See Website / Syllabus
- P2: Due next Wednesday
 - (New Project, Could be some bumps)
 - Need a Pynq
 - Groups of 2 allowed
- P3: Out now!


Failed Login & Disk Space

- If you can't log into the Linux machines:
 - It might be you are out of disk drive space

- ssh into silo/kj and do the following:


```
$ quota
```

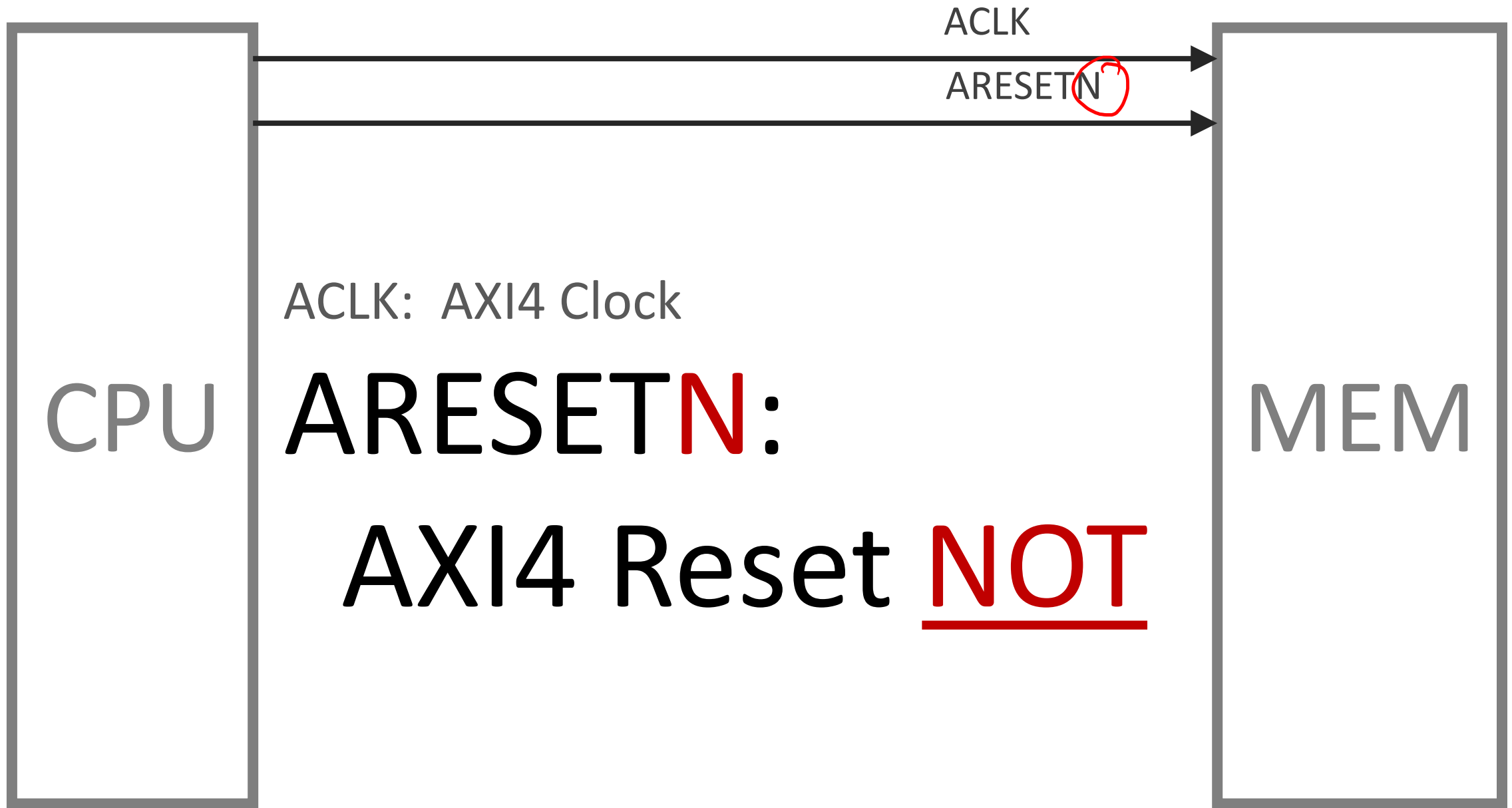
If overfull, remove some things, then try to log in again.



The Pynq

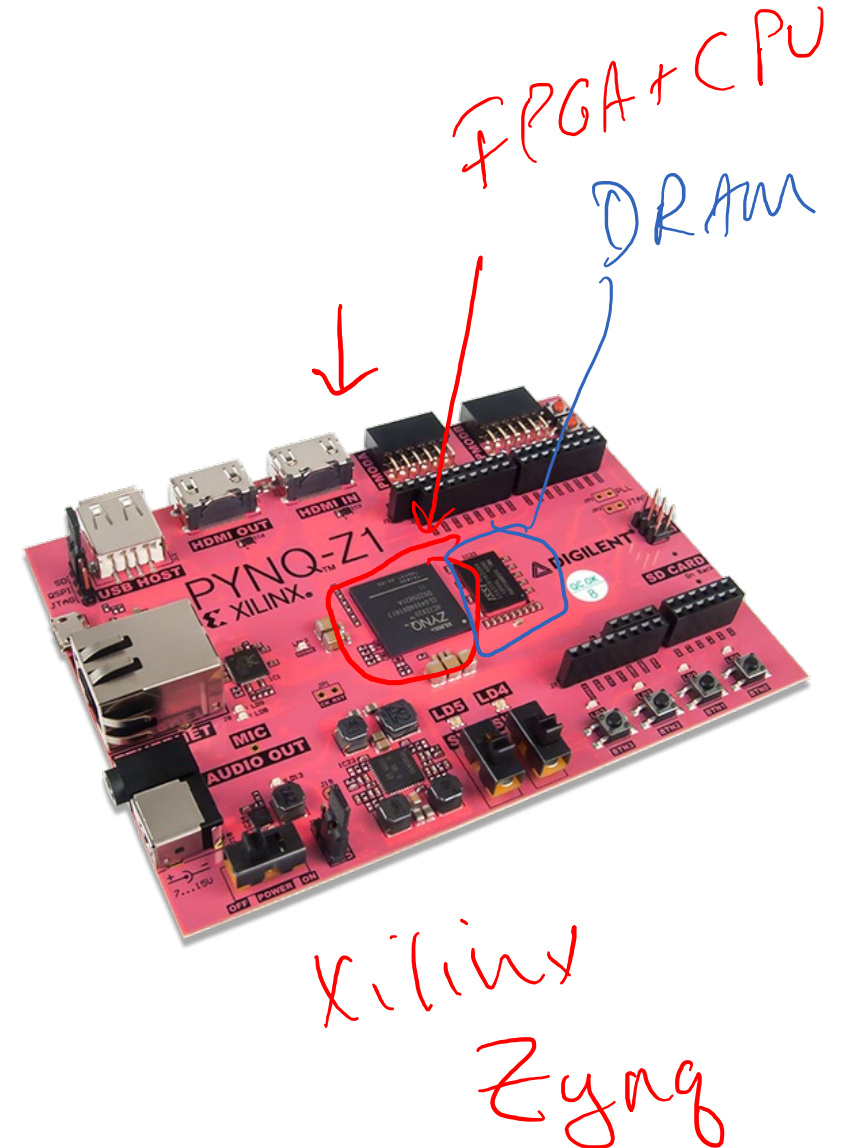- Used for P2 onward
- System-on-Chip
 - SoC - “S-O-C” or “Sock”
- Contains both FPGA and CPU
- Runs Linux + Python



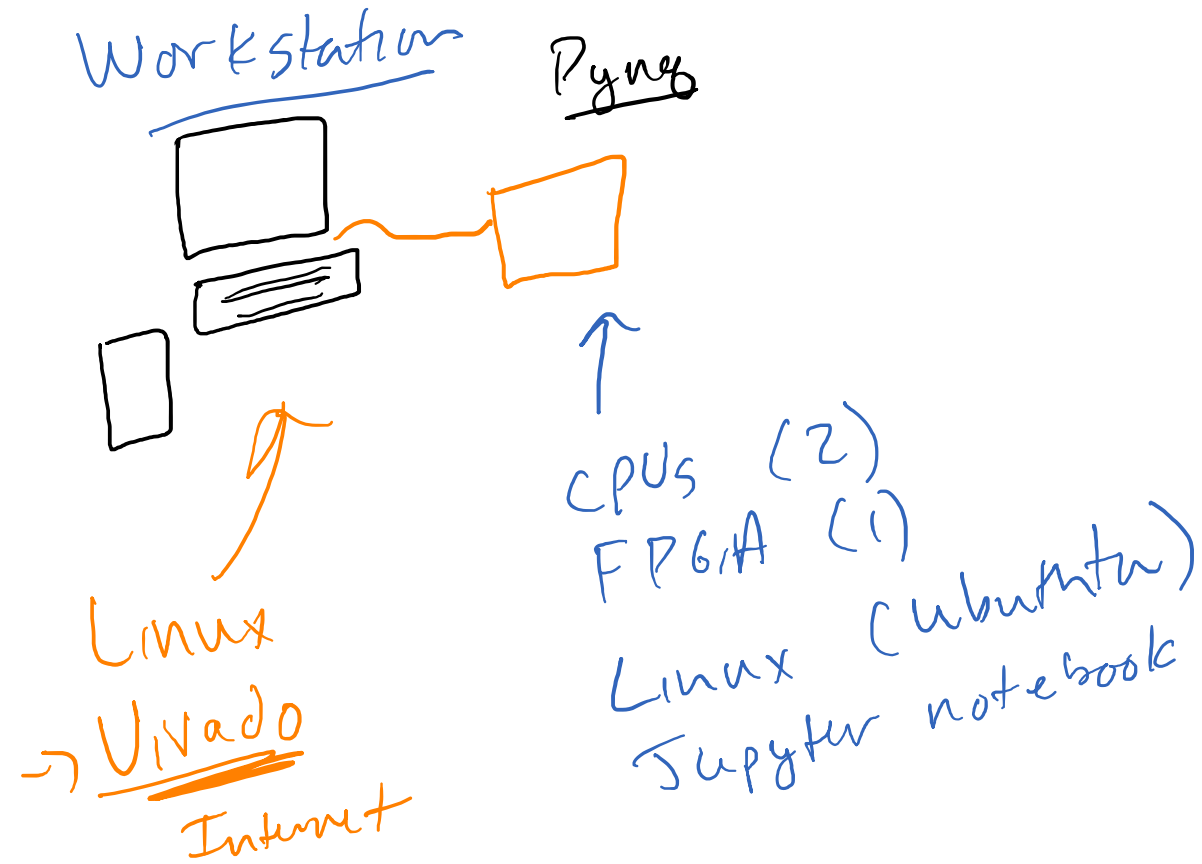

Setup Notes

- 4111 is best.
 - Everything already set up
- Can work from home
 - need Pynq networked
 - “Some” effort support
- Pure-Remote students
 - Email me.

Quick Links

[Syllabus](#)

[Lecture Slides](#)

[Other Downloads](#)

[Autograder](#)

[Canvas](#) *(Registered students only)*

Zoom *(Requires students only)*

- [Lecture](#)
- [Labs / Office Hours](#)

[Slack](#)

[Remote Setup](#)


[Pynq Network Setup](#)

FIXME: Link Broken

Let's talk P2 (and P3)

- What is EMA?
- Pynq Setup
 - The password is 'iuxilinx'
- e315helper.py
- Vivado Setup

Signal Filtering

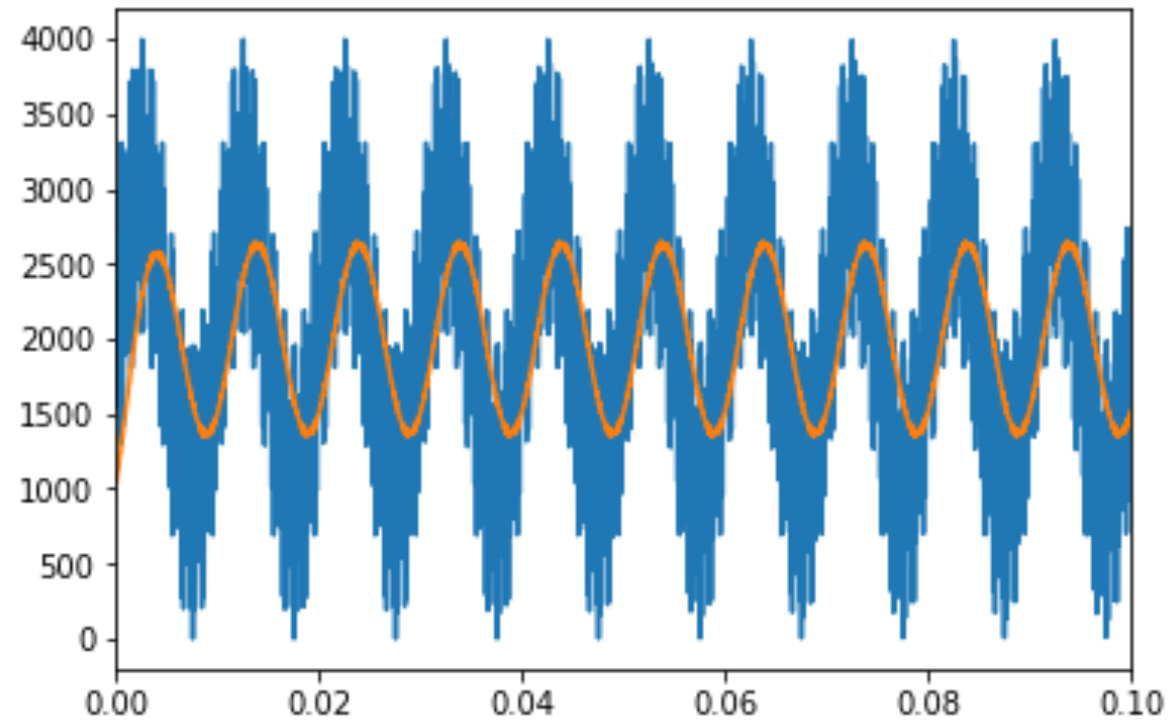


EMA Example

$$\alpha = 0.5$$

$$x = [0, 10, 0, 0, 10]$$

$$y[1] = 0$$
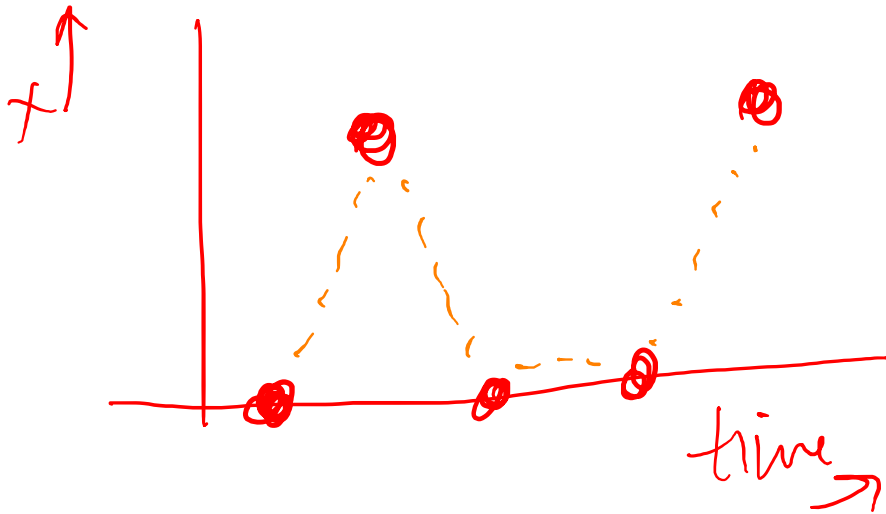
$$y[n] = \alpha x[n] + (1-\alpha) \cdot y[n-1]$$



EMA Example

$$y[1] = 0$$

$$y[n] = \alpha x[n] + (1-\alpha) \cdot y[n-1]$$

$$\alpha = 0.5$$

$$x = [0, 10, 0, 0, 10]$$

Optimizations thus far

- Algorithmic complexity
 - Function calls
 - Data structures
 - Libraries / Lower-level programming
-
- Skipped: Multicore (E201)

Did you know you can call assembly from C?

```
int popcount_asm(uint64_t num)
{
    uint64_t result;
    asm (
        "POPCNT %1, %0    \n"
        : "=r" (result)
        : "mr" (num)
        : "cc"
    );
    return result;
}
```

gcc → *asm* (underlined in red)

```
gcc -Wall -march=nehalem -o test.o test.c popcount.c
```

Optimizations thus far

- Algorithmic complexity
 - Function calls
 - Data structures
 - Libraries / Lower-level programming
 - **Hardware acceleration**
-
- Skipped: Multicore (E201)

Can we improve performance
with Python->Verilog interfacing?

Oh Yes!

We could also map popcount to hardware

```
import cPopcount  
print (cPopcount.cPopcount(0))
```

```
import hwPopcount  
print hwPopcount.hwPopcount(0))
```


First we need to understand how CPUs and hardware **communicate**.


We're going on an excursion into buses.

Buses: The hardware interface

- Standardized hardware interfaces for transferring data
- Off-chip Buses: UART, I2C, SPI, RS-485, CAN, Ethernet
- On-Chip Buses: Wishbone, AHB/APB, AXI
- We're going to study 2.
 - AXI4-Stream
 - AXI4-Lite


P3 “EMA” uses two buses to move data between CPU + hardware

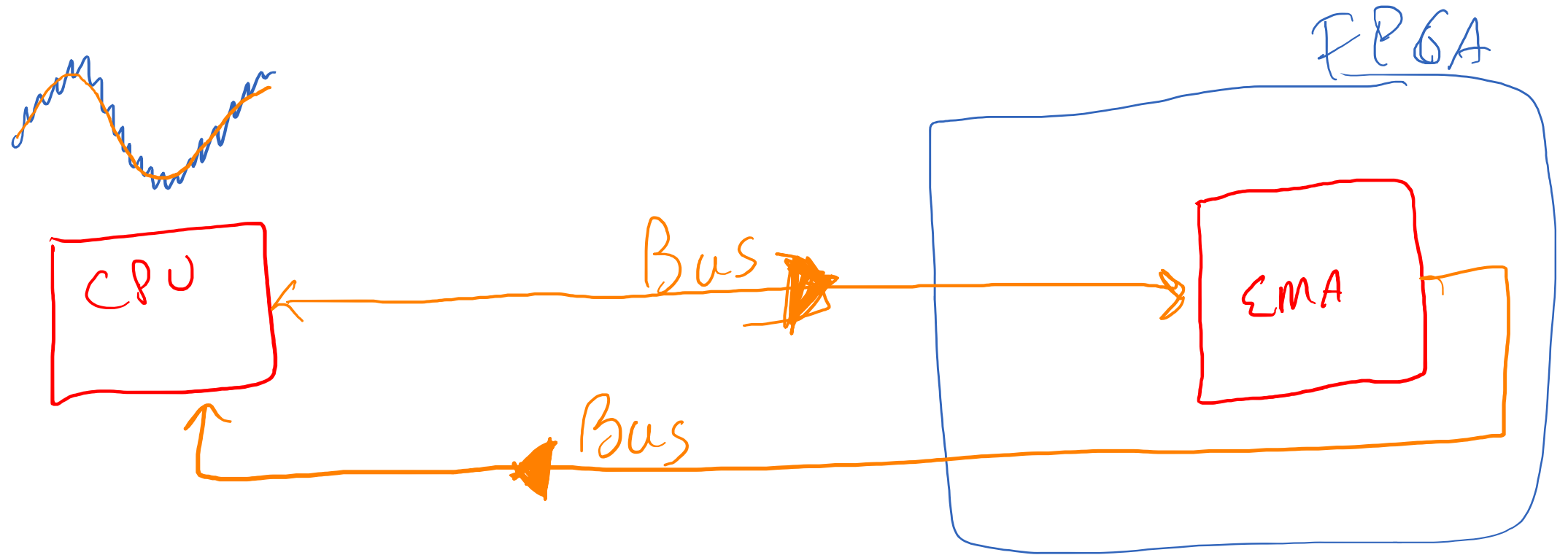P3 “EMA” uses two buses to move data between CPU + hardware



Bus terminology

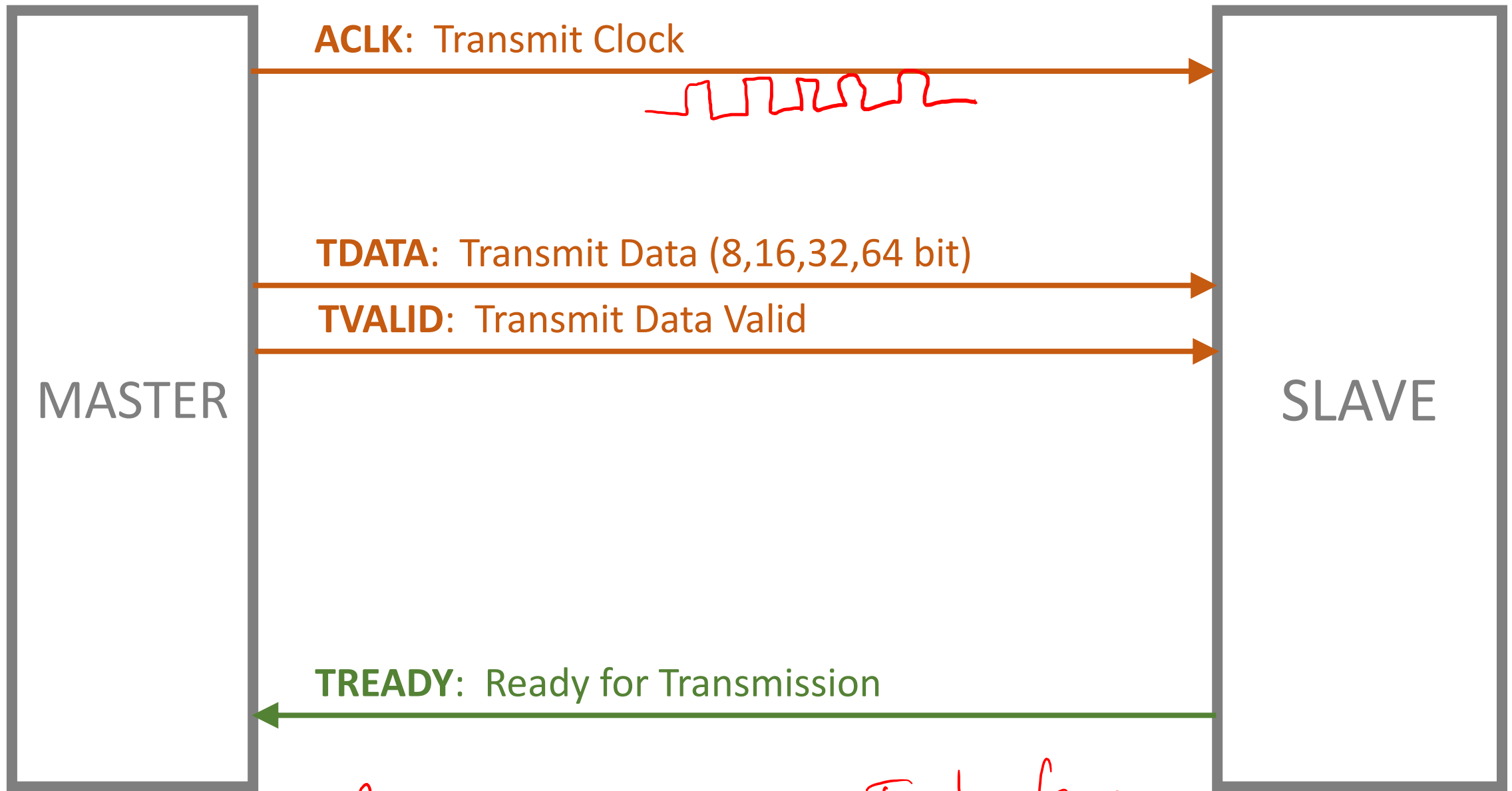- A “**transaction**” occurs between an “**initiator**” and “**target**”
- Any device capable of being an initiator is said to be a “**bus master**”
 - Usually only one bus master (single master vs. multi-master).
- A device that can only be a target is said to be a “**slave device**”.



AXI-Stream Interface

Data (**TDATA**) is only transferred when

TVALID is 1.

This indicates the **MASTER** is trying to transmit new data.


TREADY is 1.

This indicates the **SLAVE** is ready to receive the data.


If either **TVALID** or **TREADY** are 0, no data is transmitted.


If **TVALID** and **TREADY** are 1, **TDATA** is transmitted at the positive edge of **ACLK** *bigger*

Transferring data on a AXI4-Stream Bus.

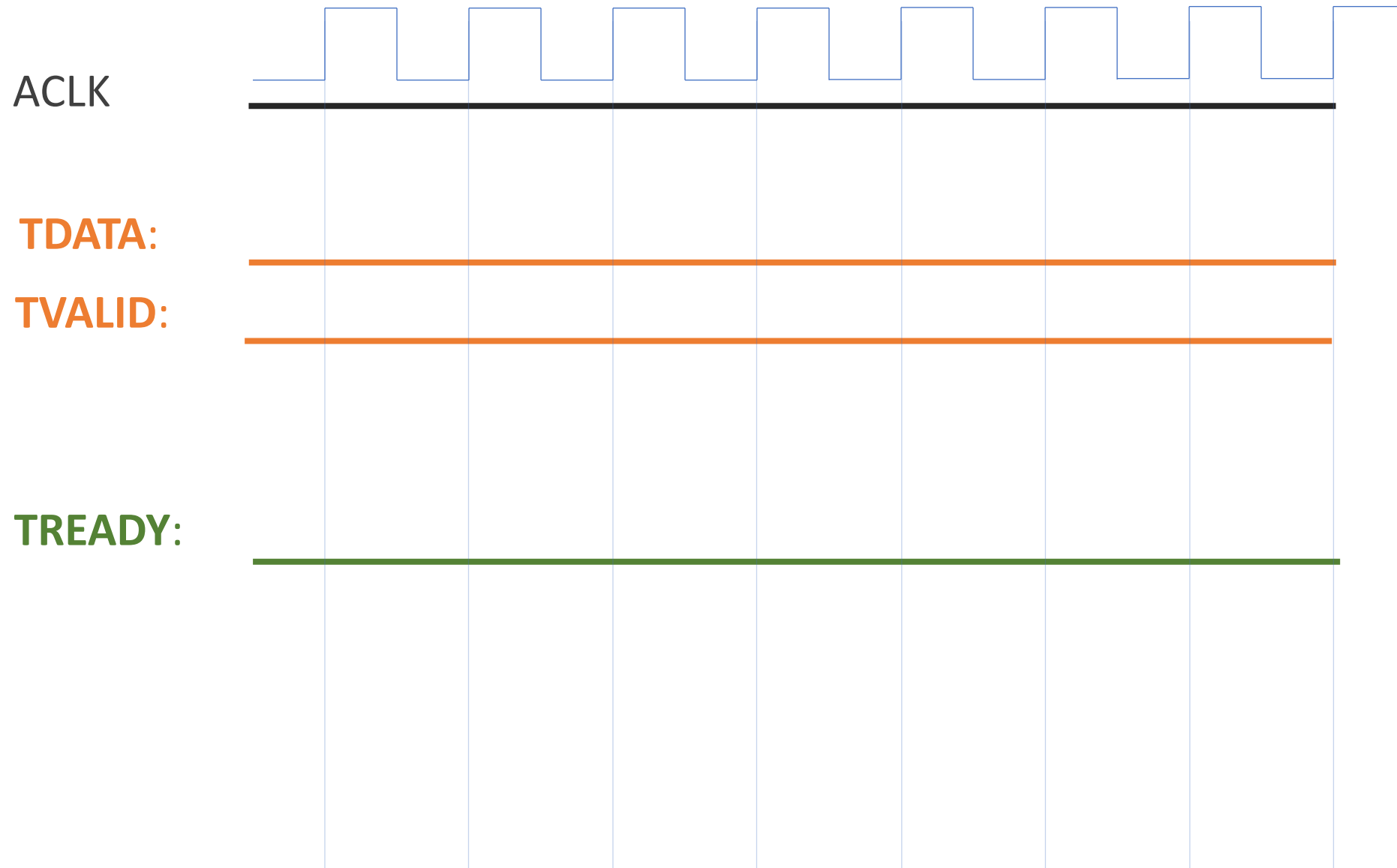

When is data transmitted?

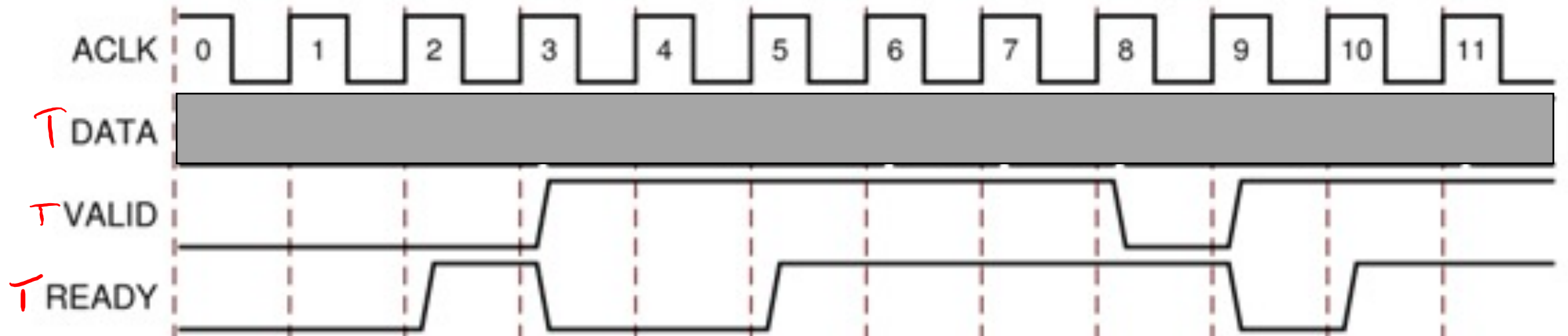


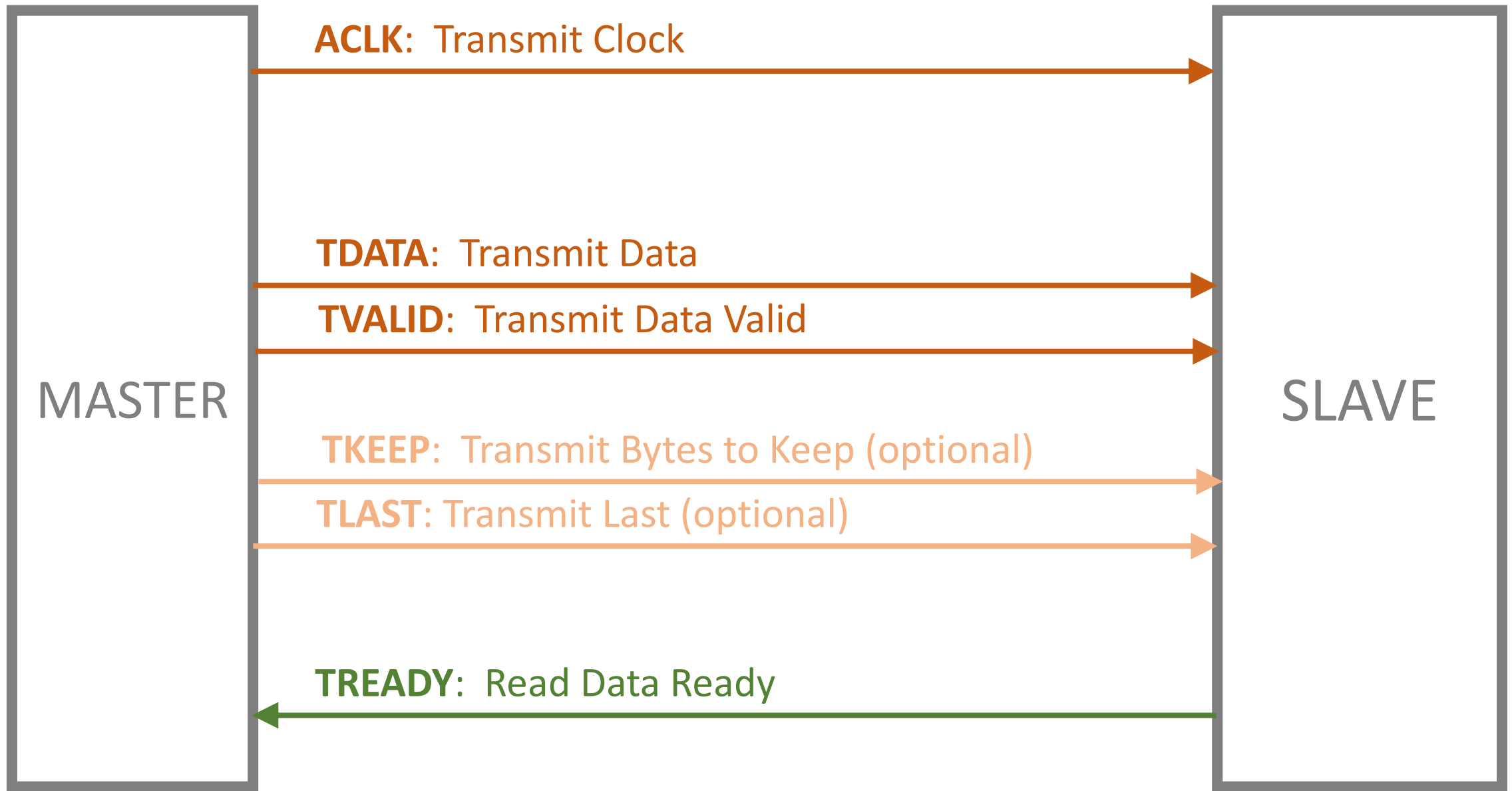

TLAST

- Special signal to indicate a group or “burst” of transmissions is complete.
- “Indicates the boundary of a packet”

Transferring data on a AXI4-Stream Bus.

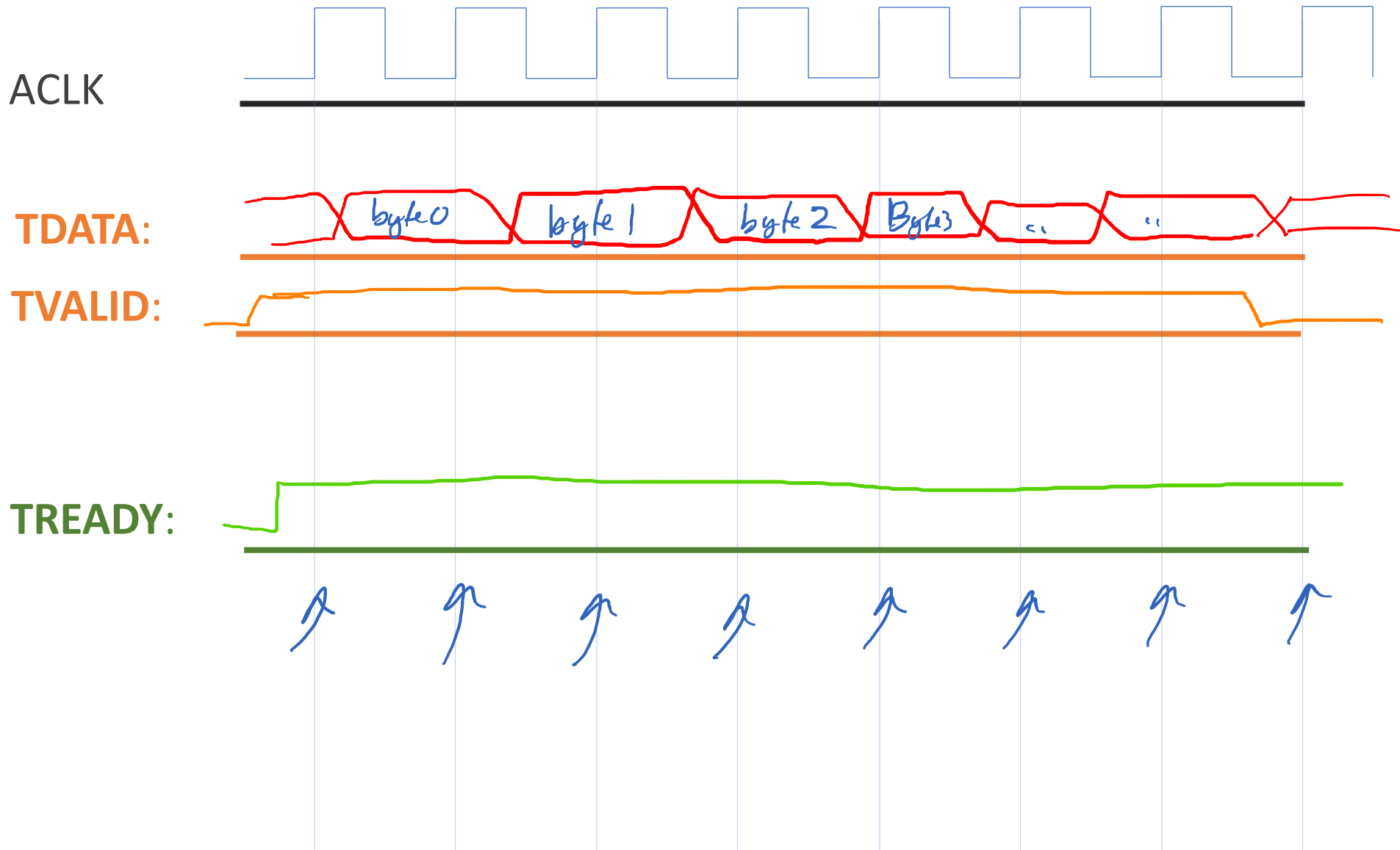



TKEEP

- What if TDATA is 32-bits (4 bytes) wide, and I want to send 6 bytes?
- **TKEEP** let's me specify which bytes to “keep”.
- **TKEEP** ==1111 -> Keep all 4 bytes (32-bits)
- **TKEEP** ==1100 -> Keep first 2 bytes (16-bit)
- **TKEEP** ==1000 -> Keep first byte (8-bit)

Transferring data on a AXI4-Stream Bus.



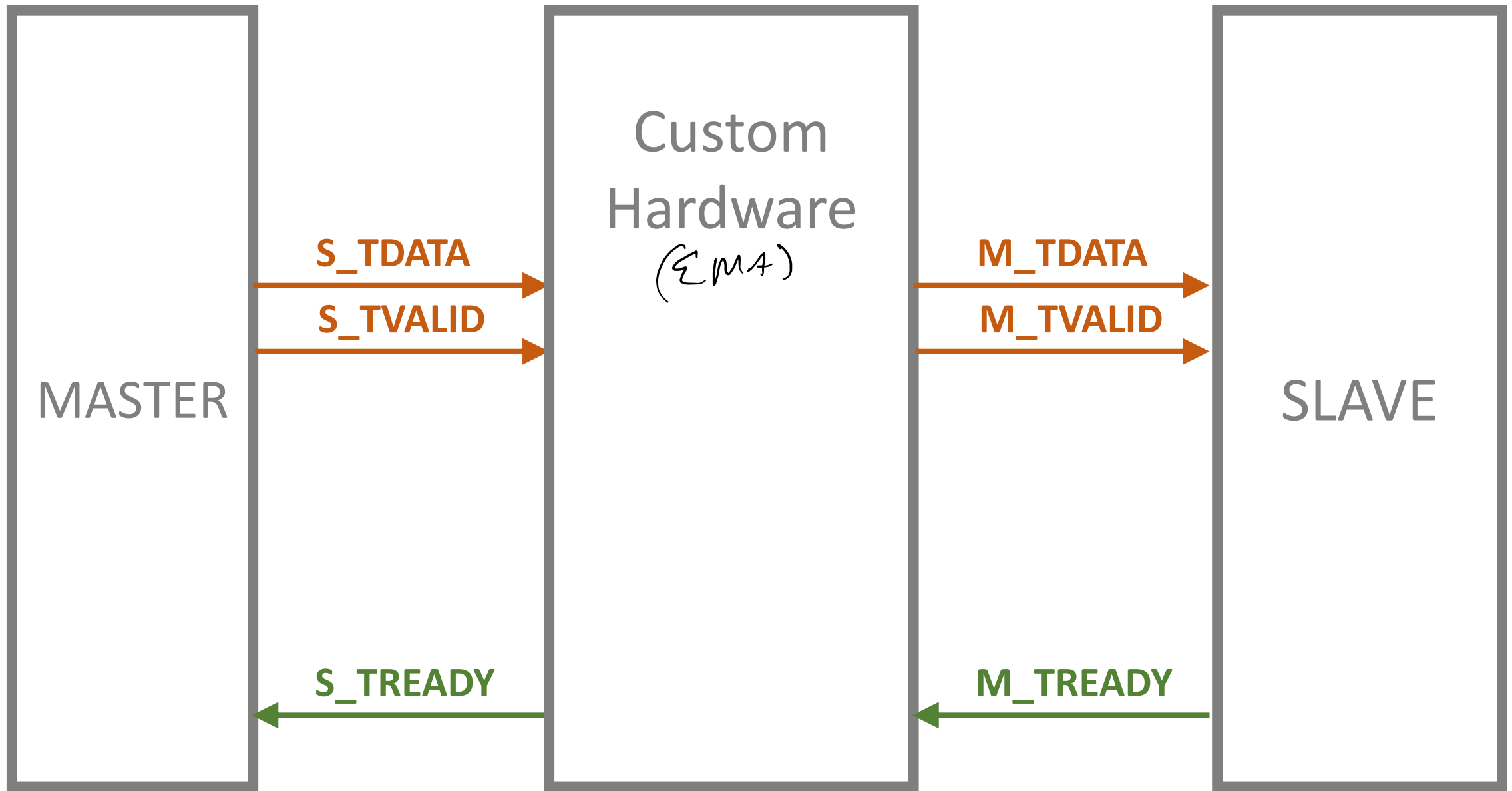


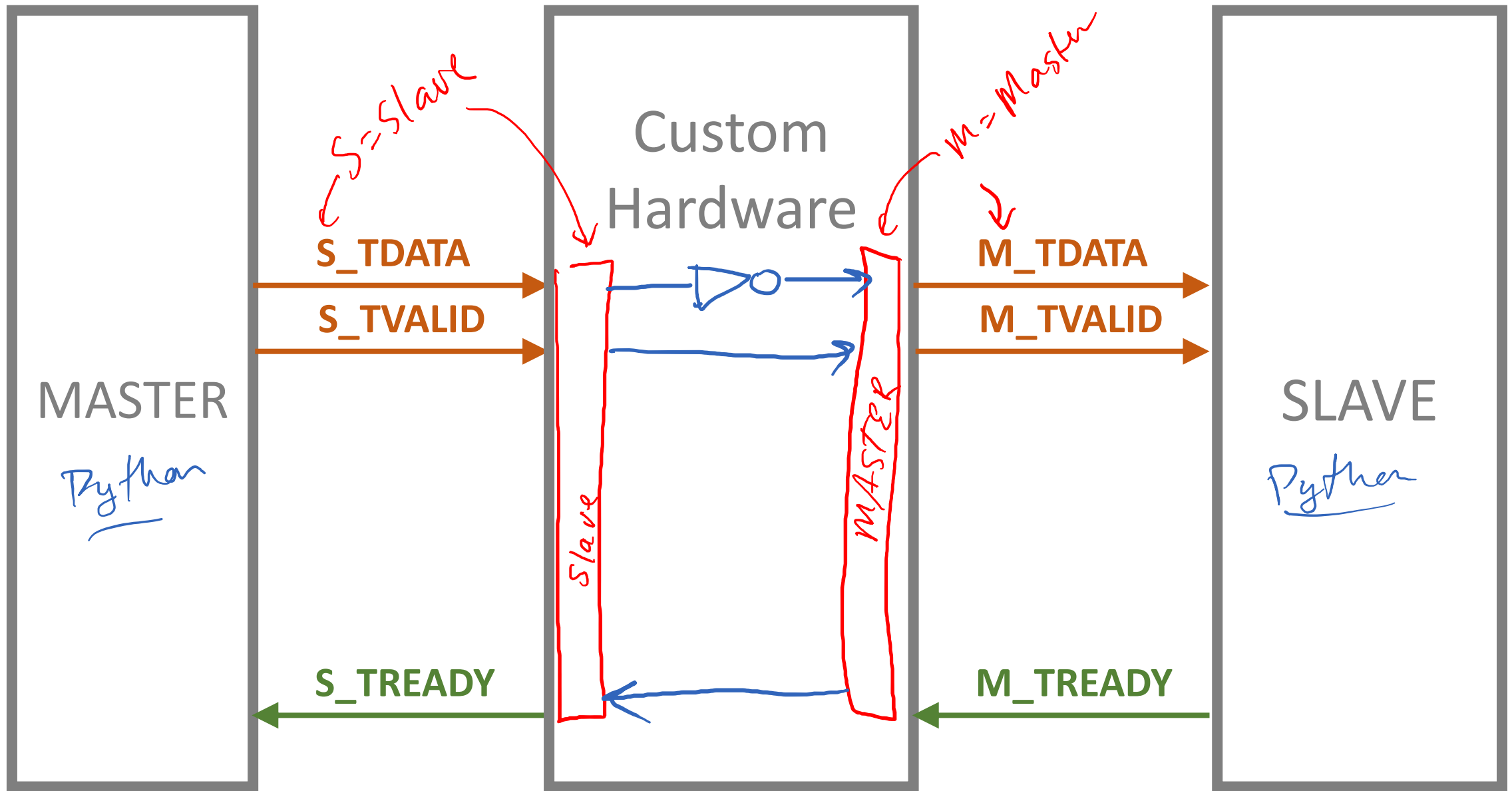

Let's build a custom block that does nothing!


```
module custom_hw (  
    input        ACLK,  
    input        ARESET,  
    input [31:0] S_TDATA,  
    input        S_TVALID,  
    output       S_TREADY,  
    output [31:0] M_TDATA,  
    output       M_TVALID,  
    input        M_TREADY  
);
```

```
endmodule
```

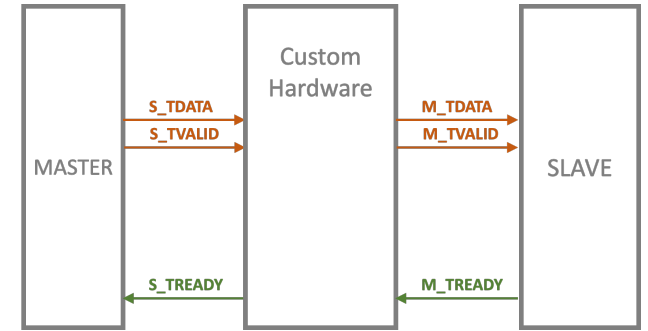

Let's build a custom block that does nothing!
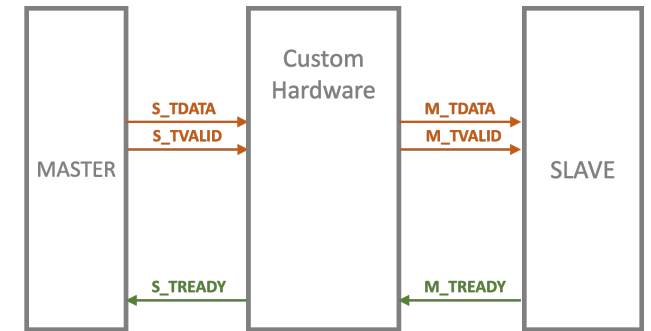
```
module custom_hw (  
    input        ACLK,  
    input        ARESET,  
    input [31:0] S_TDATA,  
    input        S_TVALID,  
    output       S_TREADY,  
    output [31:0] M_TDATA,  
    output       M_TVALID,  
    input        M_TREADY  
);  
  
    assign M_TDATA = S_TDATA;  
    assign M_TVALID = S_TVALID;  
    assign S_TREADY = M_TREADY;  
  
endmodule
```




How would I flip all the bits of TDATA?

```
module custom_hw (  
    input          ACLK,  
    input          ARESET,  
    input [31:0]   S_TDATA,  
    input          S_TVALID,  
    output         S_TREADY,  
    output [31:0] M_TDATA,  
    output         M_TVALID,  
    input          M_TREADY  
);
```

```
    assign M_TDATA = S_TDATA;  
    assign M_TVALID = S_TVALID;  
    assign S_TREADY = M_TREADY;
```

```
endmodule
```

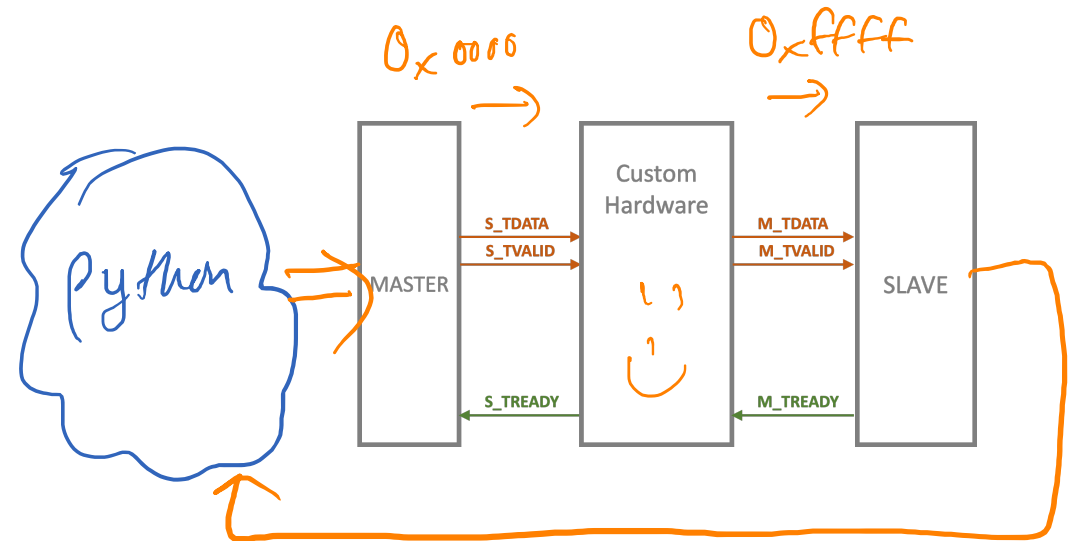



How would I flip all the bits of TDATA?

```
module custom_hw (  
    input        ACLK,  
    input        ARESET,  
    input [31:0] S_TDATA,  
    input        S_TVALID,  
    output       S_TREADY,  
    output [31:0] M_TDATA,  
    output       M_TVALID,  
    input        M_TREADY  
);
```


```
    assign M_TDATA = ~S_TDATA;  
    assign M_TVALID = S_TVALID;  
    assign S_TREADY = M_TREADY;
```

```
endmodule
```

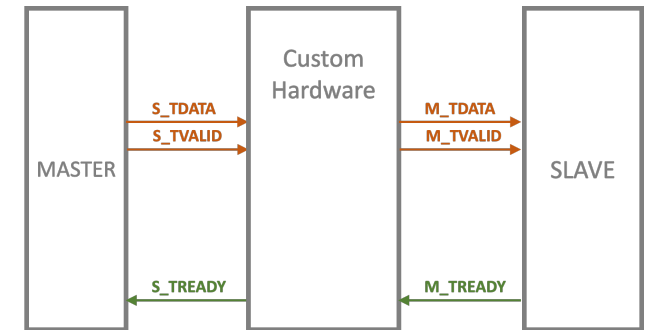

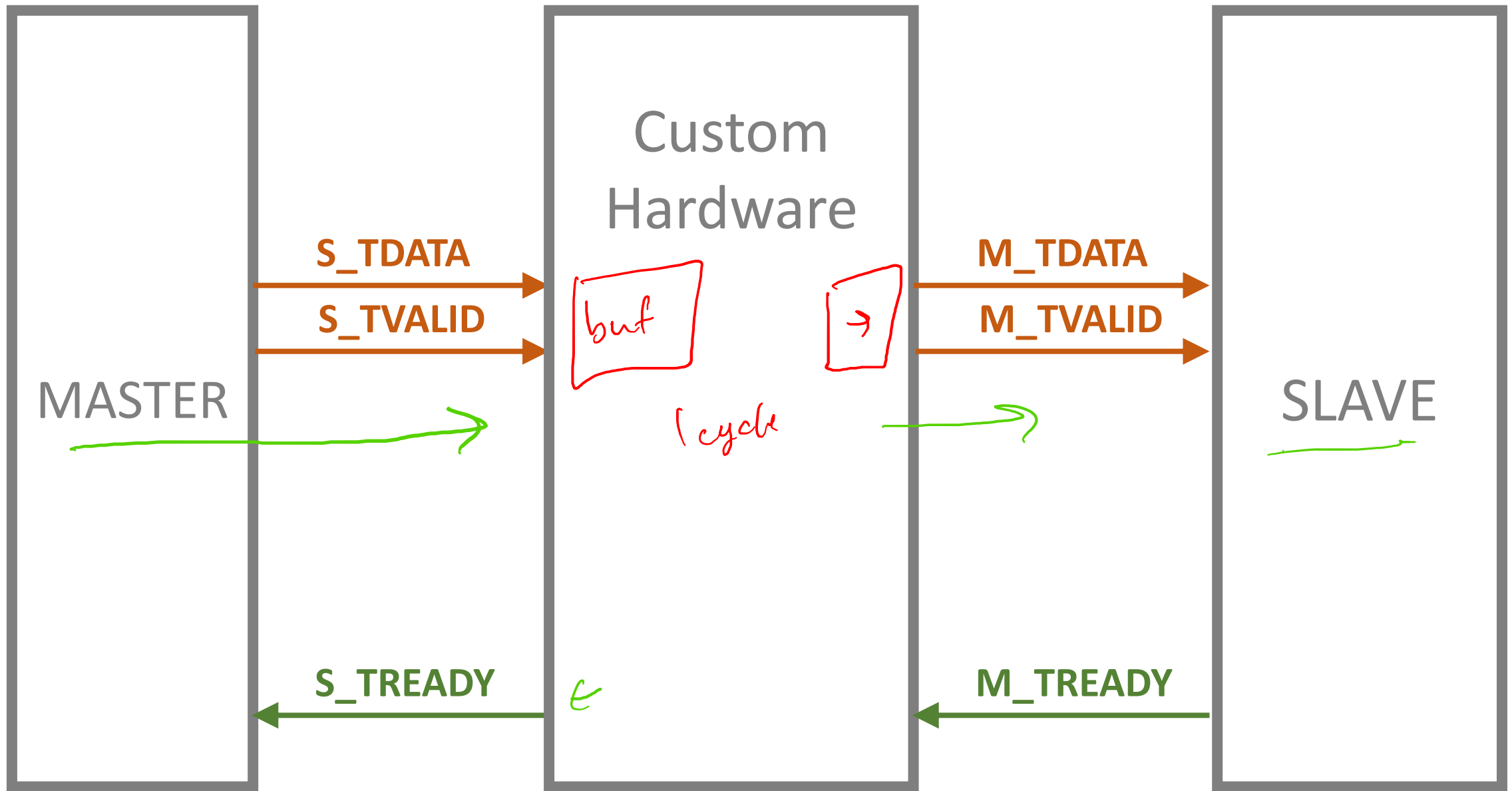


Let's build a buffer state machine.

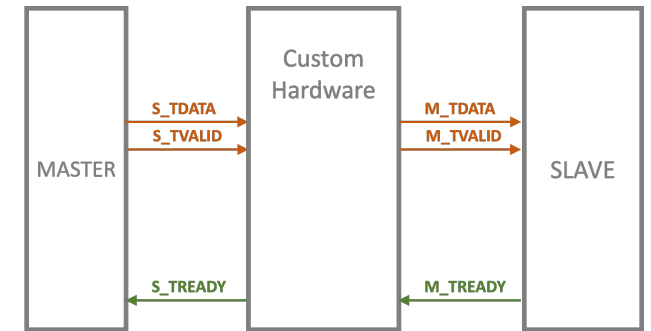


Let's build a buffer state machine.

```
module custom_hw_buf (  
    input          ACLK,  
    input          ARESET,  
    input [31:0]   S_TDATA,  
    input          S_TVALID,  
    output         S_TREADY,  
    output [31:0]  M_TDATA,  
    output         M_TVALID,  
    input          M_TREADY  
);
```

```
endmodule
```

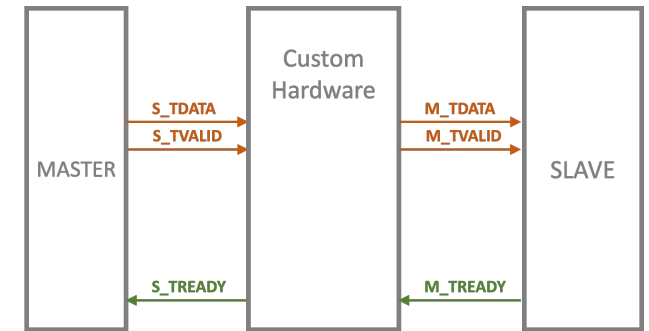

Let's build a buffer state machine.

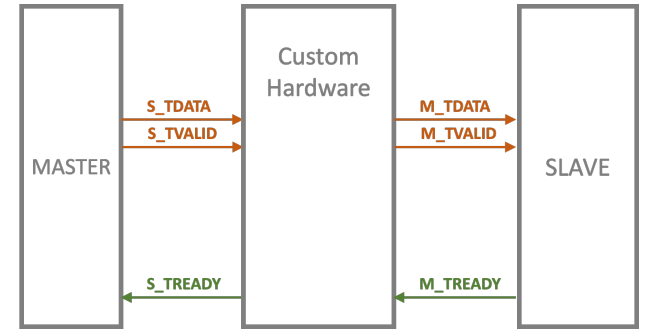

```

module custom_hw_buf (
    input          ACLK,
    input          ARESET,
    input [31:0]    S_TDATA,
    input          S_TVALID,
    output         S_TREADY,
    output [31:0]   M_TDATA,
    output         M_TVALID,
    input          M_TREADY
);

enum {S0, S1} state, nextState;
reg [31:0] nextVal;

always_ff @(posedge ACLK) begin
    if (~ARESET)begin
        state <= S0;
        M_TDATA <= 32'h0
    end else begin
        state <= nextState;
        M_TDATA <= nextVal;
    end
end

end
    
```

```

always_comb begin
    S_TREADY = 'h1;
    M_TVALID = 'h0;
    nextState = state;
    nextVal = M_TDATA;
    case(state)
        S0: begin
            if (S_TVALID) begin
                nextState = S1;
                nextVal = S_TDATA;
            end
        end
        S1: begin
            S_TREADY = 'h0;
            M_TVALID = 'h1;
            if (M_TREADY) begin
                nextState = S0;
            end
        end
    endcase
end

endmodule
    
```


Next Time

- Memory-Mapped I/O
- Memory-Mapped Buses

References

- Zynq Book, Chapter 19 “AXI Interfacing”
- [Practical Introduction to Hardware/Software Codesign](#)
 - Chapter 10
- AMBA AXI Protocol v1.0
 - http://mazsola.iit.uni-miskolc.hu/~drdani/docs_arm/AMBAaxi.pdf
- <https://lauri.võsandi.com/hdl/zynq/axi-stream.html>

03: Bus Interfaces

Engr 315: Hardware / Software Codesign
Andrew Lukefahr
Indiana University

