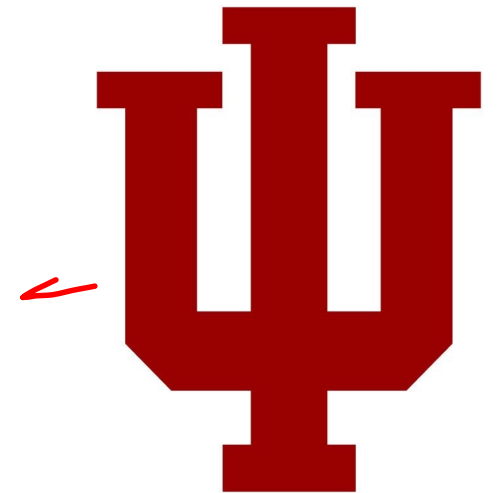


~~4.1~~ Test

06: Memory-Mapped I/O

Engr 315: Hardware / Software Codesign
Andrew Lukefahr
Indiana University



Announcements

reset → Slack

- Office Hours – See Website / Syllabus
 - *Maybe change Thursday due to conflict
- P2: Due Tonight
 - (New Project, could be some bumps)
 - Need a Pynq
 - Groups of 2 allowed
- P3: Out now!


Optimizations thus far

- Algorithmic complexity
- Removing redundant computation
- ~~• Multithreading~~
- ~~• Multiprocessing*~~
- Python/C/Asm Interfacing
- **Map to Hardware**

We could also map popcount to hardware

QMA
`import cPopcount`
`print (cPopcount.cPopcount(0))`

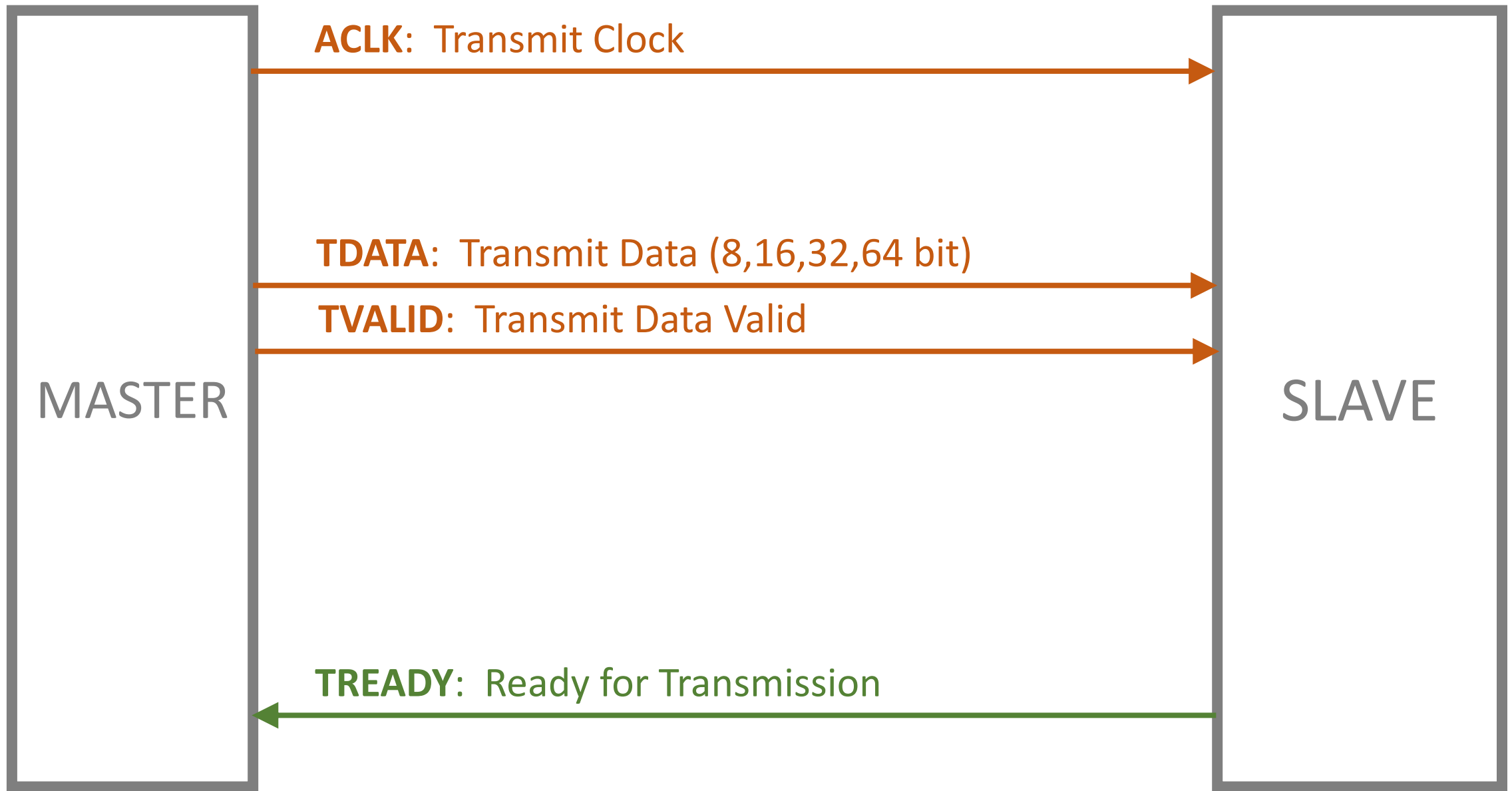QMA
`import hwPopcount`
`print hwPopcount.hwPopcount(0)`



Data (**TDATA**) is only transferred when

TVALID is 1.

This indicates the **MASTER** is trying to transmit new data.

TREADY is 1.


This indicates the **SLAVE** is ready to receive the data.

If either **TVALID** or **TREADY** are 0, no data is transmitted.

If **TVALID** and **TREADY** are 1, **TDATA** is transmitted

at the positive edge of **ACLK**

Transferring data on a AXI4-Stream Bus.

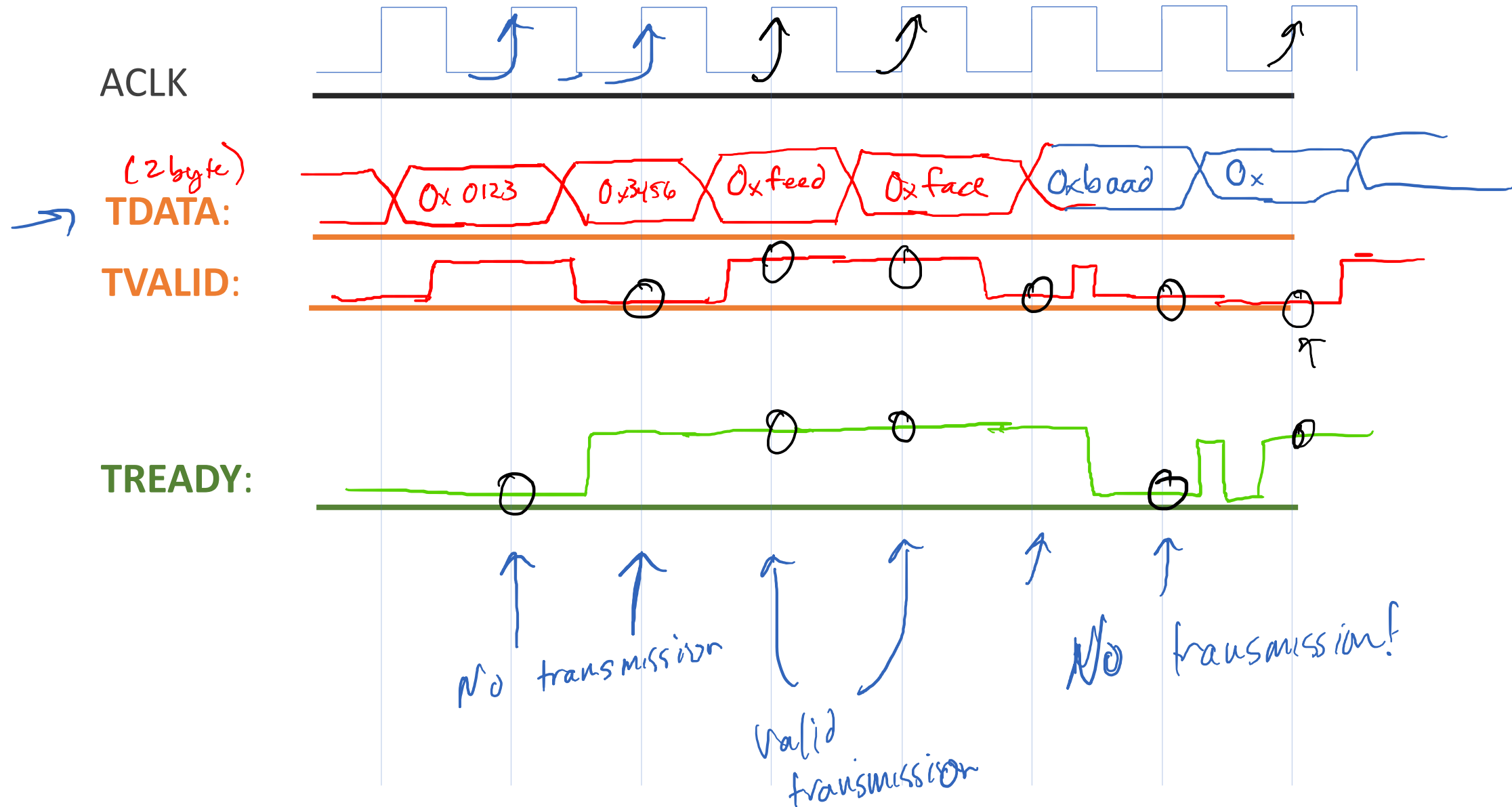


How would I flip all the bits of TDATA?



```
module custom_hw (  
    input        ACLK,  
    input        ARESET,  
    input [31:0] S_TDATA,  
    input        S_TVALID,  
    output       S_TREADY,  
    output [31:0] M_TDATA,  
    output       M_TVALID,  
    input        M_TREADY  
);
```

```
    assign M_TDATA = ~S_TDATA;  
    assign M_TVALID = S_TVALID;  
    assign S_TREADY = M_TREADY;
```


```
endmodule
```

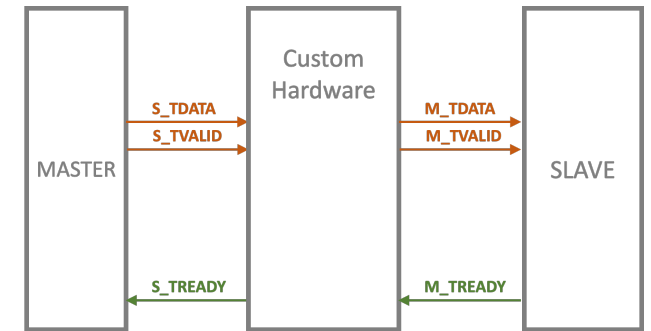

Let's build a buffer state machine.

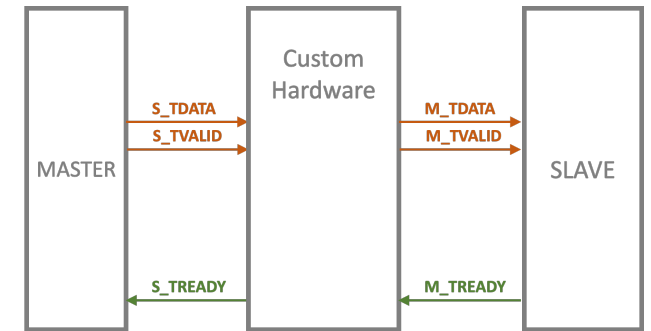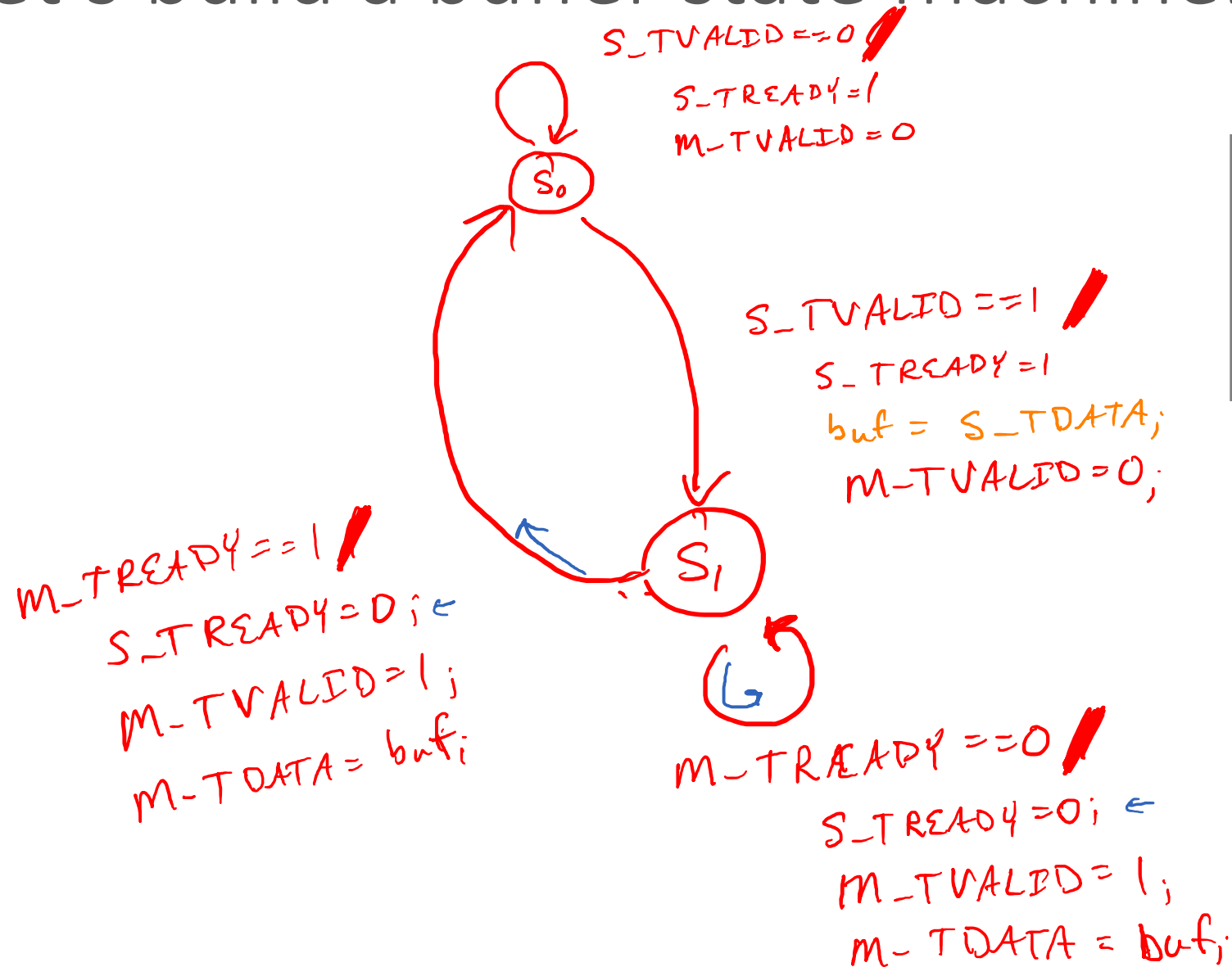

Let's build a buffer state machine.

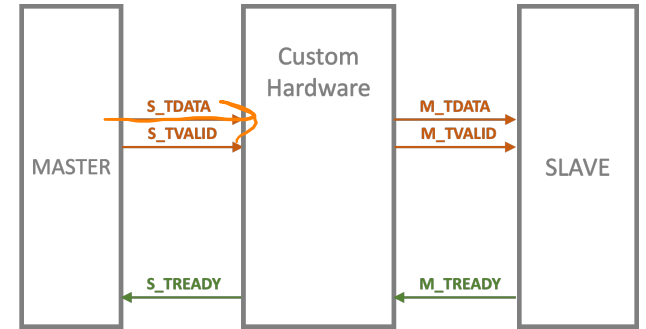

```

module custom_hw_buf (
    input        ACLK,
    input        ARESET,
    input [31:0] S_TDATA,
    input        S_TVALID,
    output       S_TREADY,
    output [31:0] M_TDATA,
    output       M_TVALID,
    input        M_TREADY
);

enum {S0, S1} state, nextState;
reg [31:0] nextVal;


always_ff @(posedge ACLK) begin
    if (ARESET)begin
        state <= S0;
        M_TDATA <= 32'h0
    end else begin
        state <= nextState;
        M_TDATA <= nextVal;
    end
end
end
    
```

```


always_comb begin
    S_TREADY = 'h1;
    M_TVALID = 'h0;
    nextState = state;
    nextVal = M_TDATA;
    case(state)
        S0: begin
            if (S_TVALID) begin
                nextState = S1;
                nextVal = S_TDATA;
            end
        end
        S1: begin
            S_TREADY = 'h0;
            M_TVALID = 'h1;
            if (M_TREADY) begin
                nextState = S0;
            end
        end
    endcase
end

endmodule
    
```

The Input/Output Problem *Pyng*

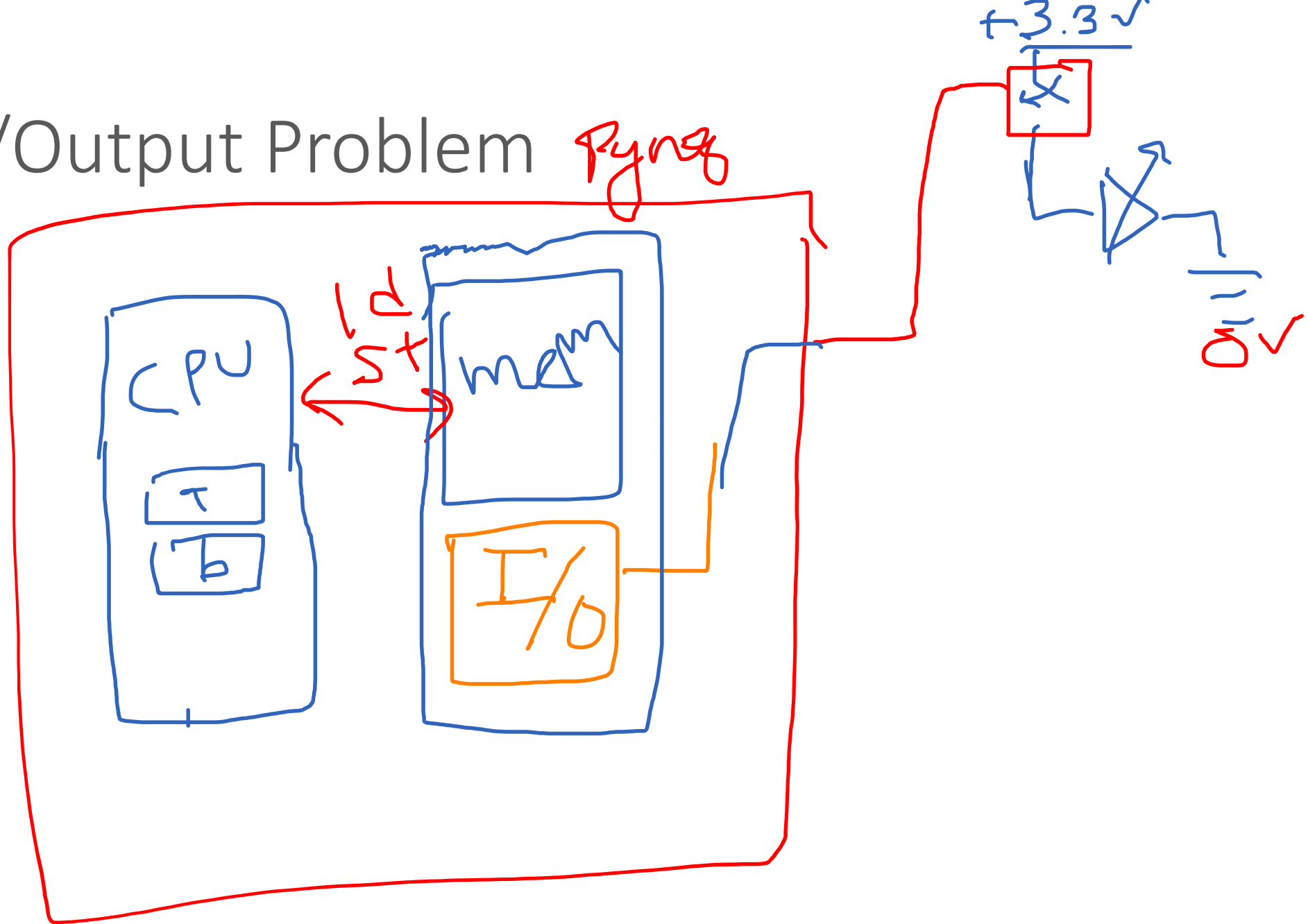

CPU + Memory

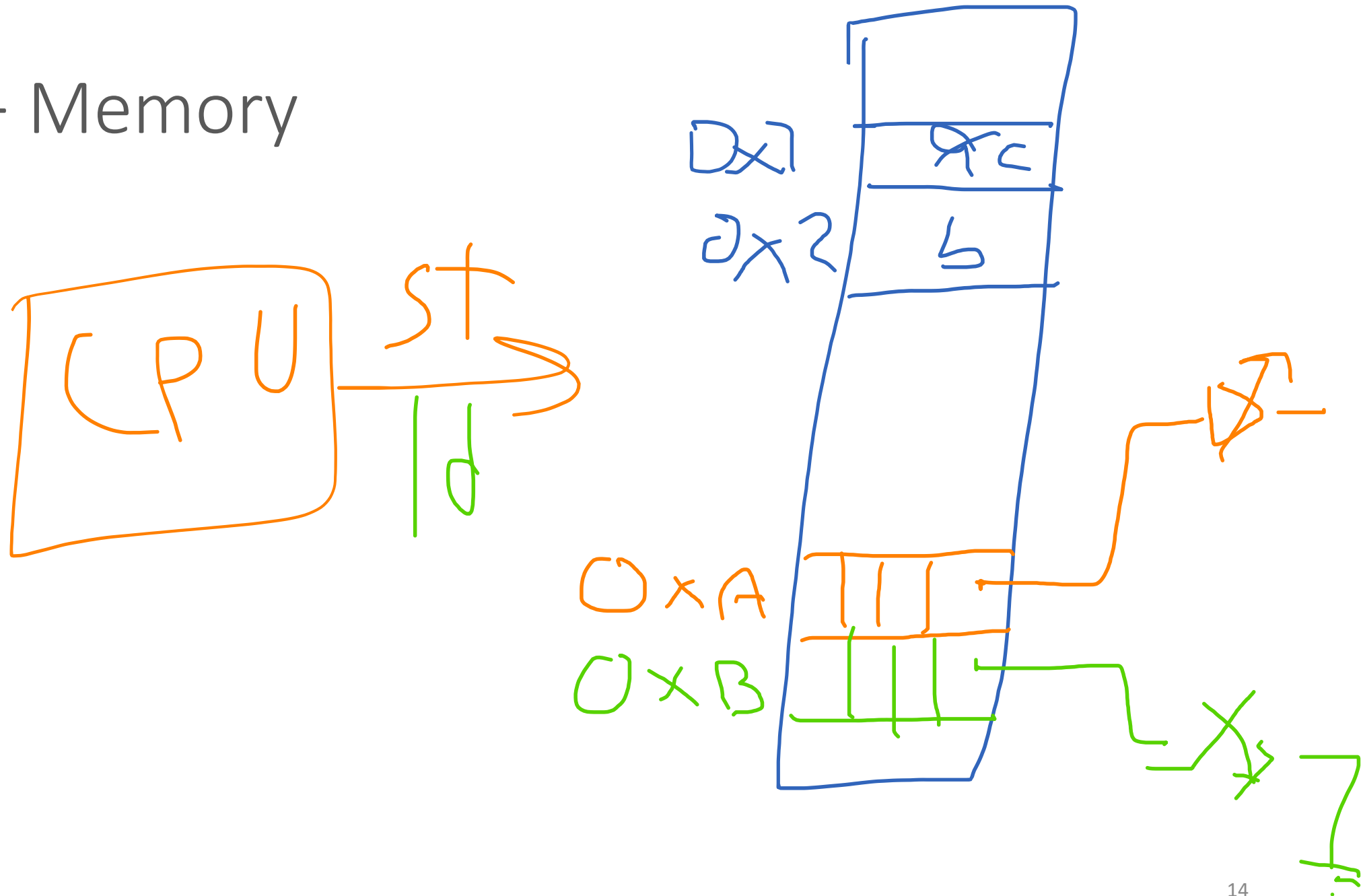

32 bit
store

0x0 → AABBC

8 bit store

0x1 → EE

32 store

0x4 → FFF

Addr	Val
0x0	AA
0x1	BB EE
0x2	CC
0x3	DD
0x4	FF
	.

Shift Addr

0000 0000
0000 0000 /

$$2^8 = 256$$

1111 1110
1111 1111

32bit
0000

0000 0000 0000 0000 0000 0000 0000 0000

$$2^{32} = \sim 4 \text{ GB}$$

$$/ 2^{64} = ?$$

32 bit

0x0


0FFF
1000
1000

FFFF
0000
FFFF



0xEFF
FFFF

CPU + Memory

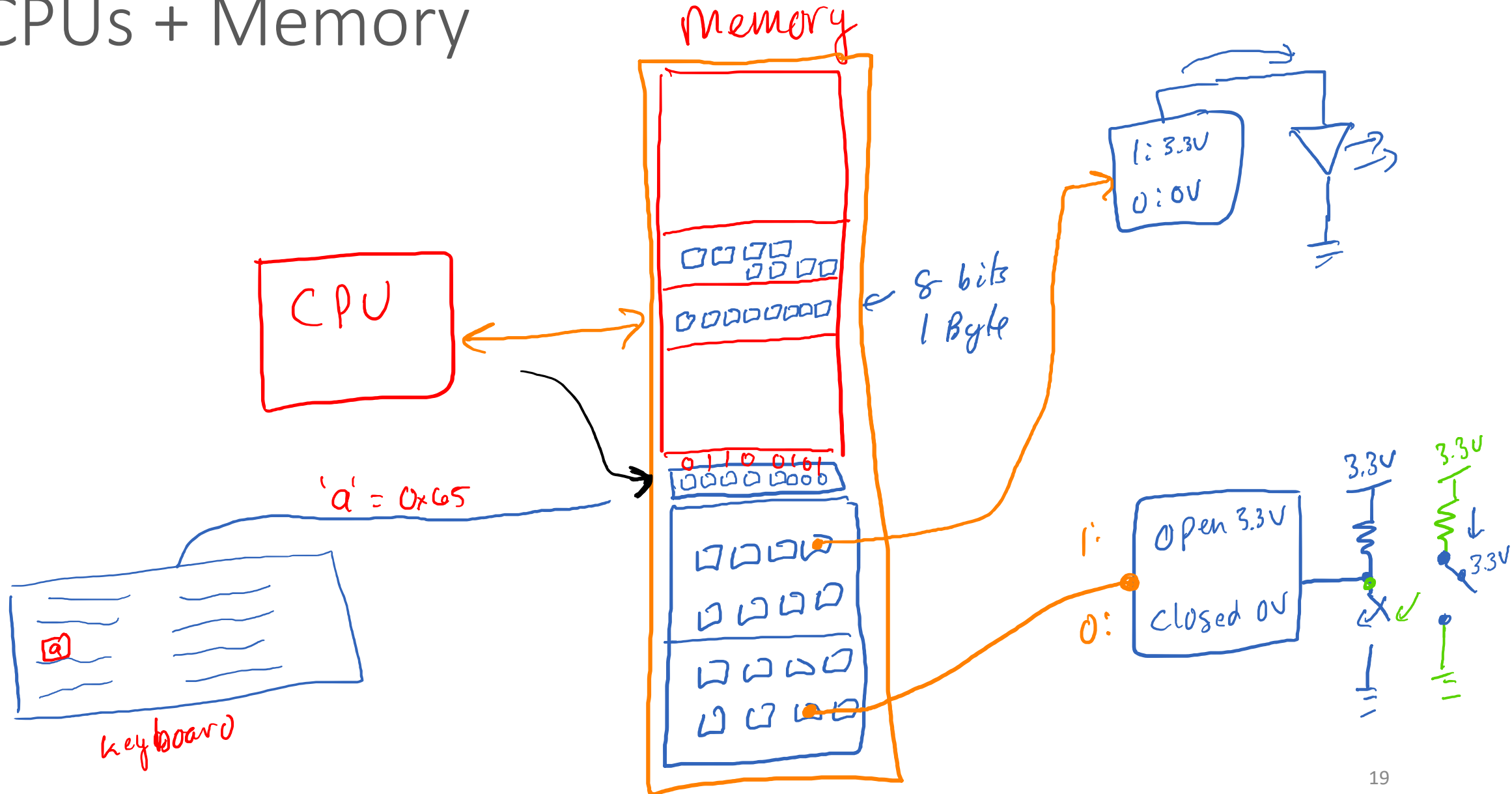

Memory-Mapped I/O

Goal: Connect I/O to memory address

Memory-Mapped I/O

- I/O devices pretend to be memory
- “Pretend Memory” I/O accessed with native CPU load/store instructions

MMIO from Assembly

- First, we need to see ARM assembly...

ARM Registers

ARM	Description	x86
R0	General Purpose	EAX
R1-R5	General Purpose	EBX, ECX, EDX, ESI, EDI
R6-R10	General Purpose	–
R11 (FP)	Frame Pointer	EBP
R12	Intra Procedural Call	–
R13 (SP)	Stack Pointer	ESP
R14 (LR)	Link Register	–
R15 (PC)	<- Program Counter / Instruction Pointer ->	EIP
CPSR	Current Program State Register/Flags	EFLAGS

ARM Instructions

Instruction	Description	Instruction	Description
MOV	Move data	EOR	Bitwise XOR
MVN	Move and negate	LDR	Load
ADD	Addition	STR	Store
SUB	Subtraction	LDM	Load Multiple
MUL	Multiplication	STM	Store Multiple
LSL	Logical Shift Left	PUSH	Push on Stack
LSR	Logical Shift Right	POP	Pop off Stack
ASR	Arithmetic Shift Right	B	Branch
ROR	Rotate Right	BL	Branch with Link
CMP	Compare	BX	Branch and eXchange
AND	Bitwise AND	BLX	Branch with Link and eXchange
ORR	Bitwise OR	SWI/SVC	System Call


ARM Load + Store

LDR R2, [R0]
found in R0.

@ [R0] - origin address is the value

STR R2, [R1]
found in R1.

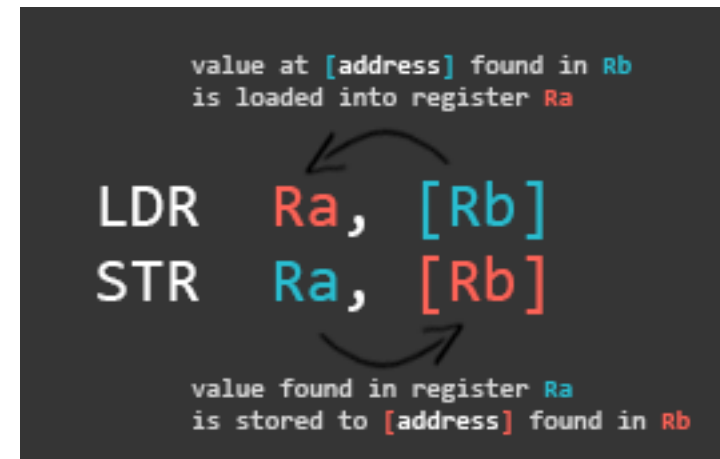
@ [R1] - destination address is the value




MMIO Store from ASM (ARM)

MMIO Store from ASM (ARM)
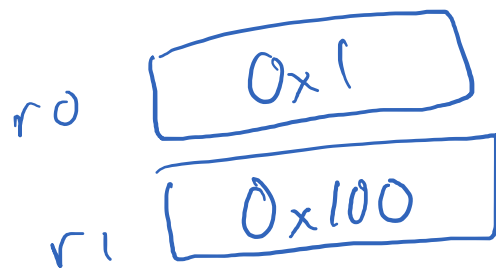
```
mov r0, 0x1  
mov r1, [0x100]  
str r0, [r1]
```




Store `0x1` to `mem[0x100]`

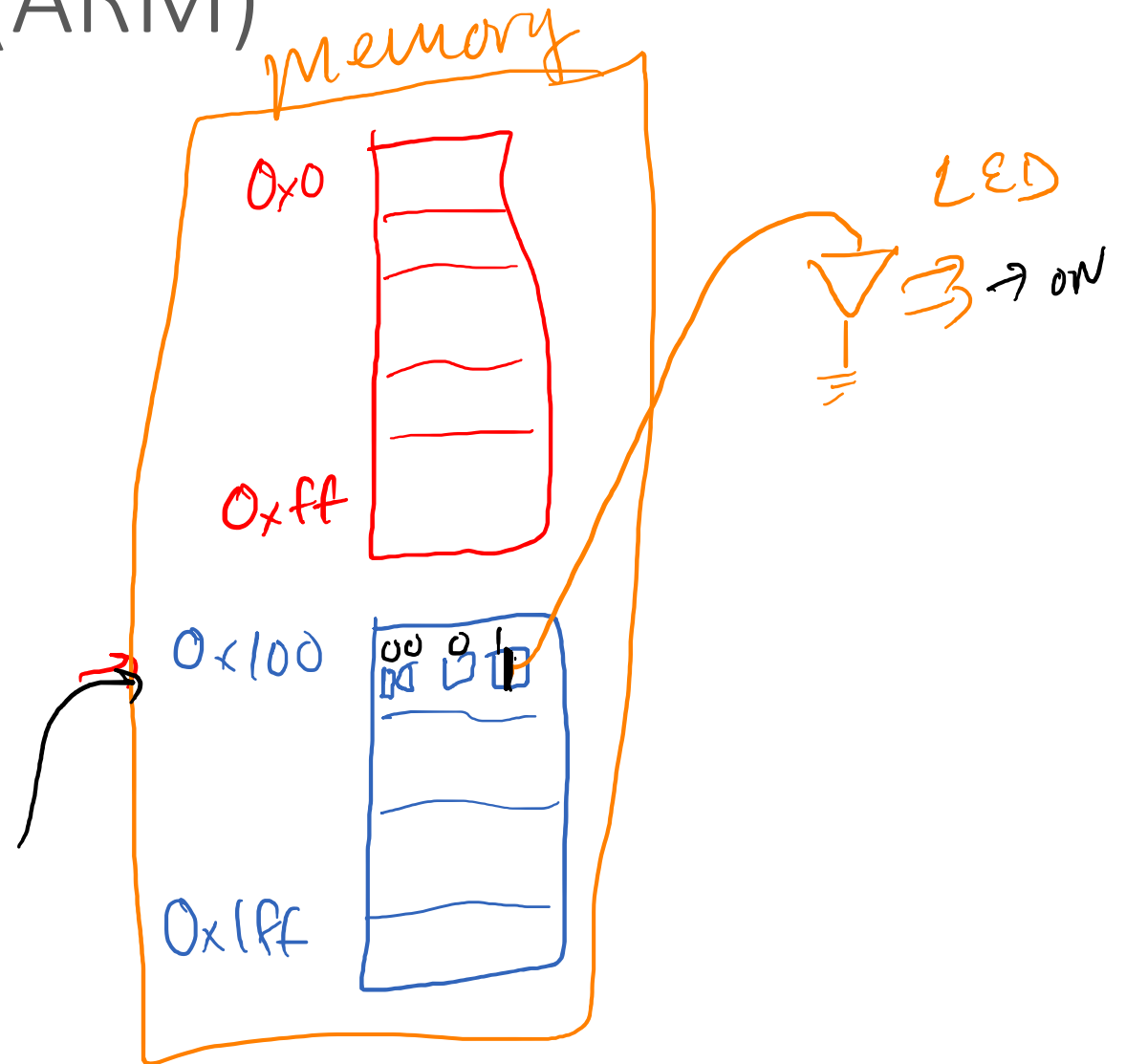

MMIO Load from ASM (ARM)

MMIO Load from ASM (ARM)

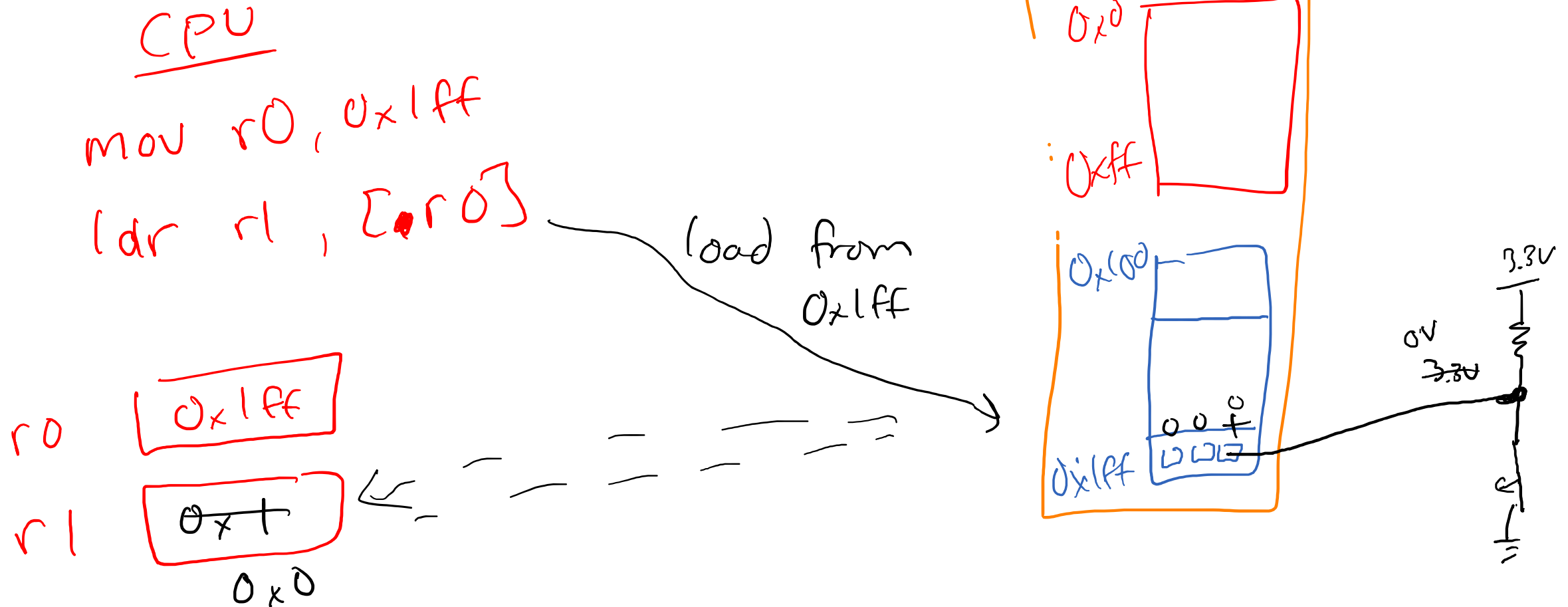

MMIO Store from C

```
#define LED_ADDR 0x1000xffff  
uint32_t * LED_REG = (uint32_t *) (LED_ADDR);  
*LED_REG = 0x1;
```

LR 100

0x100 0x1

MMIO Store from C

```
#define LED_ADDR 0xfffff
uint32_t * LED_REG = (uint32_t *) (LED_ADDR);
*LED_REG = 0x1;
```

MMIO Load from C

STOP

MMIO Load from C

```
#define SW_ADDR 0xfffe
uint32_t * SW_REG = (uint32_t *) (SW_ADDR);
int y = (*SW_REG);
```

cast value as an address

reference to get memory at the address

Problem: Does `quit` ever change here?
Do I need to recompute `(!quit)`?
(-O3 edition)

```
int y = 0;

int quit = y;
while(!quit)
{
    //more code
    quit = y;
}
```

Problem: Does `quit` ever change here?
Do I need to recompute `(!quit)`?
(-O3 edition)

```
int y = 0;
int quit = y;
while(!quit)
{
    //your code
    quit = y; //What if y is a switch?
}
```


What about here?

```
int y = 0;
uint32_t * SW_REG = &y;

int quit = (*SW_REG);
while(!quit)
{
    //your code
    quit = (*SW_REG);
}
```

What about here?

```
int y = 0;
uint32_t * SW_REG = &y;

int quit = (*SW_REG);
while(!quit)
{
    //your code
    quit = (*SW_REG);
}
```

Use `volatile` for MMIO addresses!

```
#define SW_ADDR 0xfffe
volatile uint32_t * SW_REG = (uint32_t * SW_ADDR);

int quit = (*SW_REG);
while(!quit)
{
    //more code
    quit = (*SW_REG);
}
```

volatile Variables

- `volatile` keyword tells compiler that the memory value is subject to change randomly.
- Use `volatile` for all MMIO memory. The values change randomly!

Use `volatile` for
all MMIO memory.

What happens here?

```
#include <stdio.h>
#include <inttypes.h>

#define REG_FOO 0x40000140

int main () {
    volatile uint32_t *reg = (uint32_t *) (REG_FOO);
    *reg += 3;

    printf("0x%x\n", *reg); // Prints out new value
}
```

Let's find out...

```
vi test.c
```


```
arm-none-eabi-gcc -o test.o test.c -g
```

```
-O1 --specs=nosys.specs
```


```
arm-none-eabi-objdump -DS test.o > test.dis
```

What do the CPU and Memory need to communicate?

or I/O

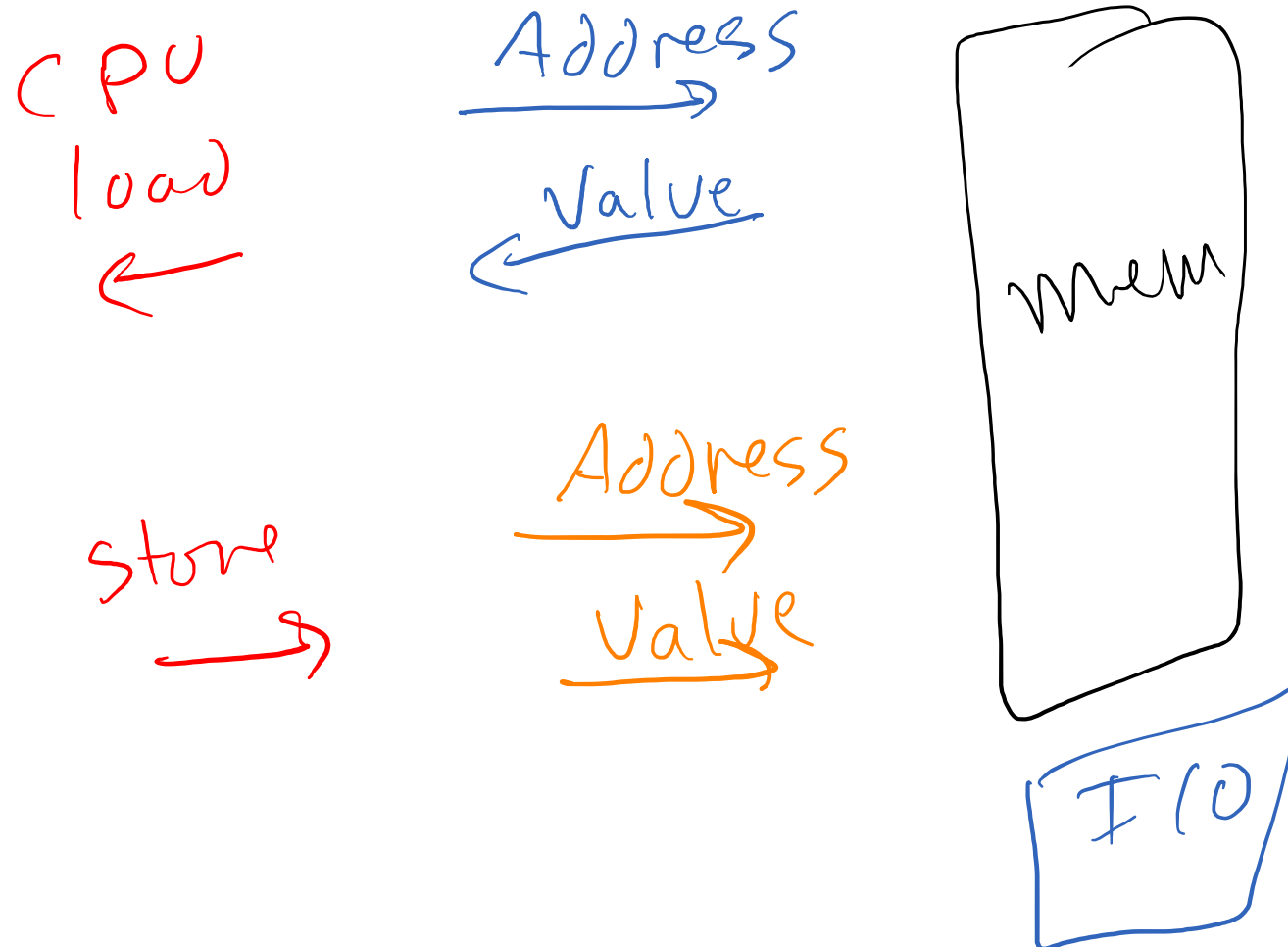

The System Bus

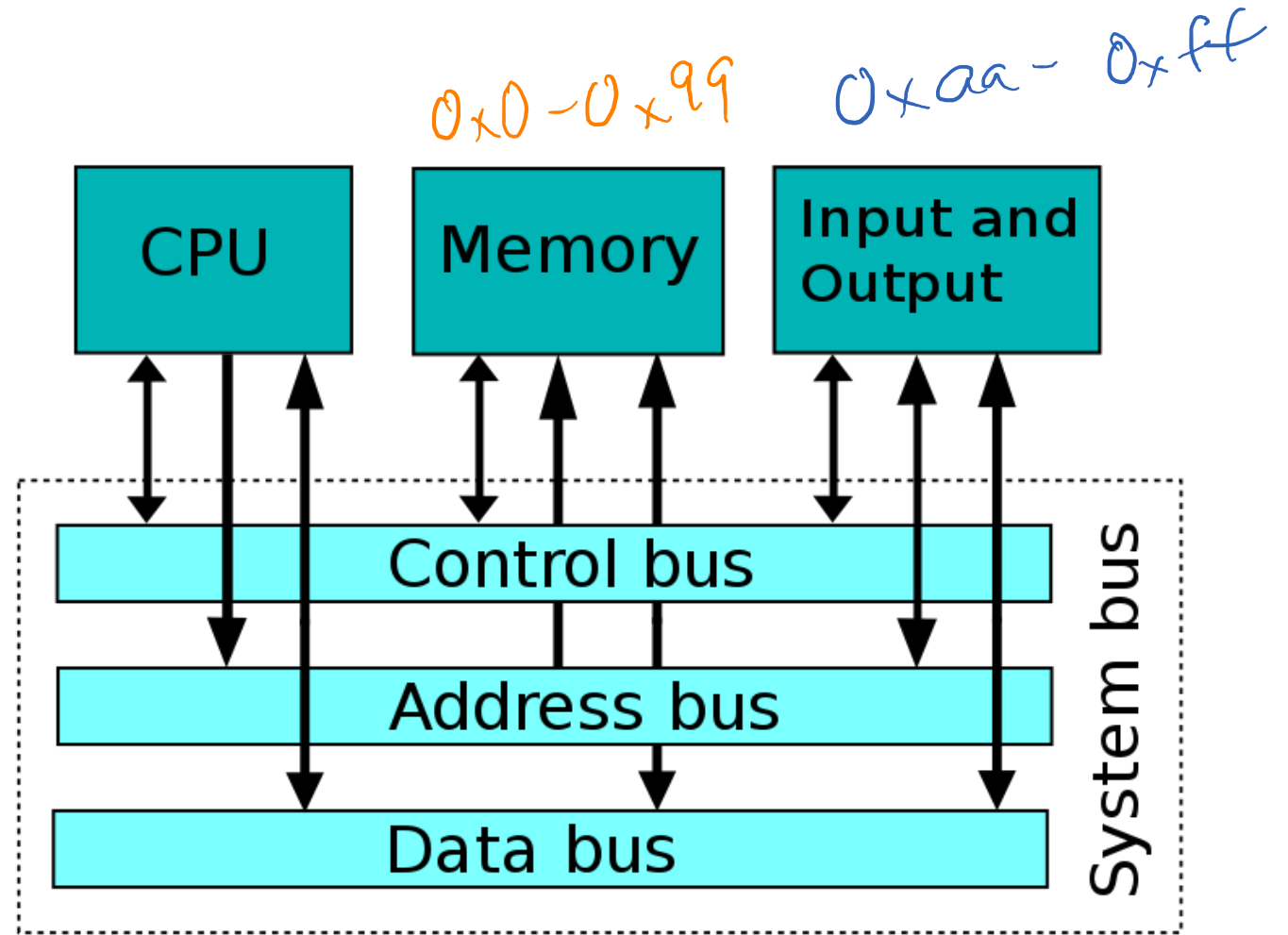

Next Time

- Combine MMIO + AXI Bus

06: Memory-Mapped I/O

Engr 315: Hardware / Software Codesign
Andrew Lukefahr
Indiana University

